
John Danielle T Castor

20


11-24-23


Project 4

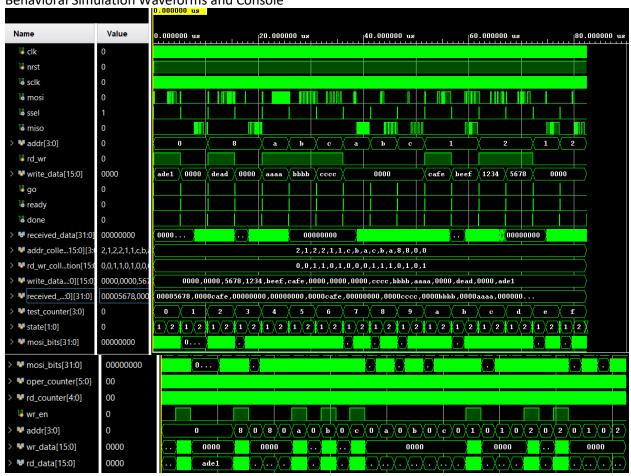
Behavioral Simulation Waveforms and Console






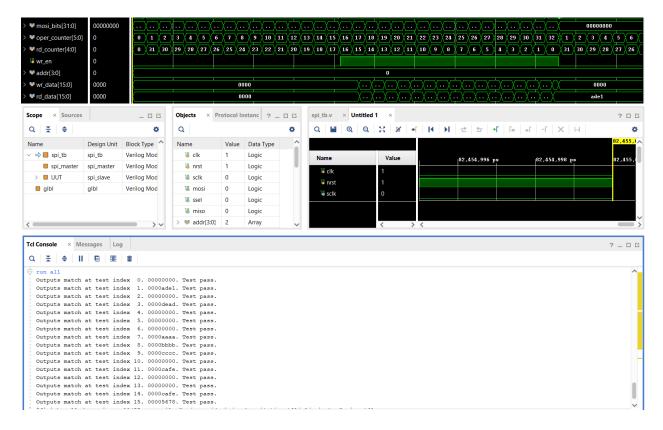

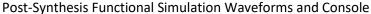

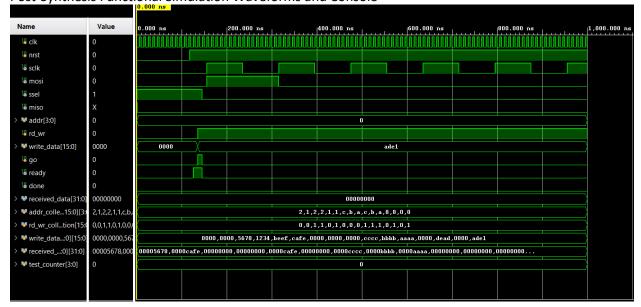

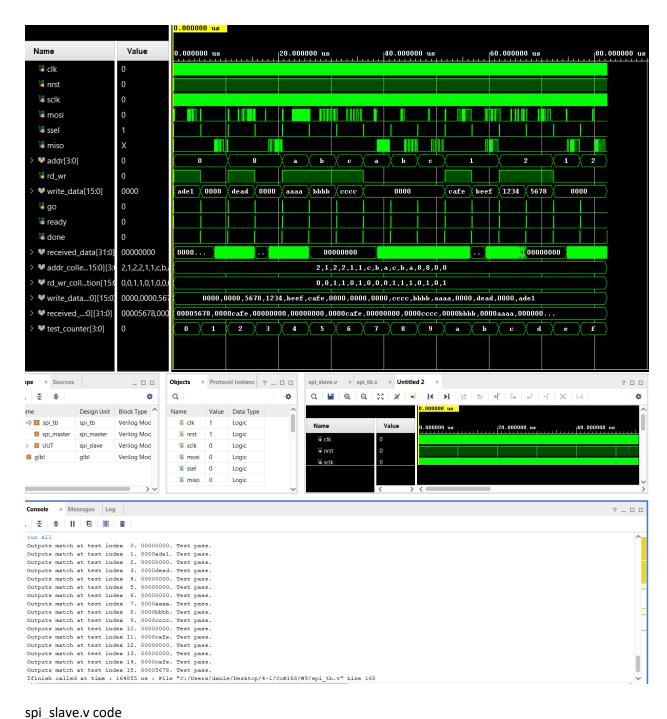

```
`timescale 1ns / 1ps

module spi_slave
(
    input clk,
    input nrst,
    input sclk,
```

input mosi, input ssel,

```
output reg miso
  );
reg [15:0] wr_data;
wire [15:0] rd data;
reg [3:0] addr;
reg wr_en;
// write your other internal signals here
reg [1:0] state;
reg sclk_prev;
reg ssel_prev;
reg [31:0] mosi_bits;
reg [5:0] oper_counter;
reg [4:0] rd_counter;
reg wr_checker;
// register file instantiation
regfile regfile(
  .clk(clk),
  .nrst(nrst),
  .wr_en(wr_en),
  .addr(addr),
  .wr_data(wr_data),
  .rd_data(rd_data)
);
// you should only use posedge clk. Don't use posedge sclk, or negedge sclk!
always@(posedge clk or negedge nrst) begin
  if (!nrst) begin
    miso \le 0;
    wr_data <= 16'b000000000000000;
    addr <= 4'b0000;
    wr_en <= 0;
    state <= 2'b00;
    sclk_prev <= 0;
    ssel_prev <= 0;
    mosi bits <= 32'h00000000;
    oper counter <= 6'b000000;
    rd_counter <= 6'b100000;
    wr_checker <= 0;
  end else begin
    sclk_prev <= sclk; //01- posedge, won't update right away
    if (sclk prev == 0 \& sclk == 1) begin \frac{1}{0}
      mosi_bits <= {mosi_bits[30:0], mosi};
      oper counter <= oper counter + 1;
```

```
rd_counter <= rd_counter - 1;
    end
    if (state == 2'b00) begin
      ssel prev <= ssel;
      if (ssel prev == 1 & ssel == 0) begin //Ssel becomes 0 from 1
        state <= 2'b01;
        mosi bits <= 32'h00000000;
        oper_counter <= 6'b000000;
         rd counter <= 6'b100000;
      end
      else
        state <= 2'b00;
    end
    else if (state == 2'b01) begin
      if (oper counter < 6'b010000)
        state <= 2'b01;
      else if (oper_counter == 6'b010000) begin //Counter = 16, 16th bit
        state <= 2'b10;
        wr en <= mosi bits[15];
        addr <= mosi bits[3:0];
        if (sclk_prev == 0 & sclk == 1 & mosi_bits[15] == 1)
           wr data <= {wr_data[14:0], mosi};</pre>
        else if (sclk_prev == 0 & sclk == 1 & mosi_bits[15] == 0)
           miso <= rd data[rd counter];
      end
    end
    else if (state == 2'b10) begin //Obtain 17th bit
      if (wr_en == 1) begin //Write
        if (oper_counter < 6'b100000 & oper_counter > 6'b010000) begin
           if (sclk_prev == 1 & sclk == 0)
             wr data <= {wr data[14:0], mosi};</pre>
           state <= 2'b10;
        else if (oper_counter == 6'b100000 & oper_counter > 6'b010000) begin //Counter = 32, 32nd bit,
bit31
           if (sclk prev == 0 \& sclk == 1)
             wr_data <= {wr_data[14:0], mosi};
           ssel_prev <= ssel;
           state <= 2'b11;
        end
      end
      else if (wr en == 0) begin //Read
        if (oper counter < 6'b100000 & oper counter > 6'b010000) begin
           //if (sclk prev == 1 & sclk == 0)
```

```
miso <= rd_data[rd_counter];
          state <= 2'b10;
        end
        else if (oper_counter == 6'b100000 & oper_counter > 6'b010000) begin
          //if (sclk prev == 0 & sclk == 1)
             miso <= rd_data[rd_counter];
          ssel_prev <= ssel;
          state <= 2'b11;
        end
      end
    end
    else if (state == 2'b11) begin
      ssel_prev <= ssel;
      if (wr_en == 1) begin
        if (sclk_prev == 1 & sclk == 0)
          wr_data <= {wr_data[14:0], mosi};
      end
      else if (wr_en == 0) begin
        if (sclk_prev == 1 & sclk == 0)
          miso <= rd_data[rd_counter];
      end
      if (ssel_prev == 0 & ssel == 1) begin //Ssel becomes 1 from 0
        state <= 2'b00;
        miso \le 0;
        wr_data <= 16'b000000000000000;
        addr <= 4'b0000;
        wr_en <= 0;
        state <= 2'b00;
        sclk_prev <= 0;
        mosi_bits <= 32'h00000000;
        oper_counter <= 6'b000000;
        rd counter <= 6'b100000;
      end
      else
        state <= 2'b11;
    end
  end
endmodule
```

end